

JAN 22, 2014

TRANSDUCERS

↳ TEMP

↳ THERMOCOUPLE

↳ SEEBECK EFFECT

↳ USING 2 DIFF. METALS @ 2 DIFF JUNCTIONS, A ~~CURRENT~~ CHANGE OF TEMP CAN INDUCE A CURRENT

↳ USED TO MEASURE TEMP BASED ON CURRENT

↳ USES COLD REFERENCE FOR CALIBRATION

↳ TC EXAMPLE:

A TYPE J TC HAS 0°C REF. A VOLTAGE OF 4.617mV IS READ. WHAT IS THE ACTUAL TEMP @ THE JUNCTION?

↳ USE TYPE J CONVERSION TABLE

(ROWS TELL 10 'S, COLUMNS TELL 1 'S BASED ON V)

TYPE J \rightarrow REF = 20°C $V = 36.69\text{mV}$


ADD V FROM 20°C TO 36.69mV TO FIND

PROPER V FOR 0°C REFERENCE

$$\therefore V = 37.709\text{mV}$$

$$\text{TEMP} = 677^{\circ}\text{C}$$

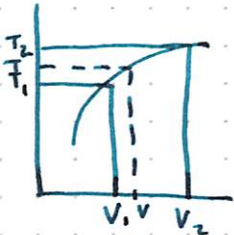TO FIND A NON-LISTED VOLTAGE, FIND THE TEMPS BOUNDING & USE LINEAR INTERPOLATION



$$T(V) = T_1 + (T_2 - T_1) \frac{(V - V_1)}{(V_2 - V_1)}$$

$$\frac{(V - V_1)}{(V_2 - V_1)} = \frac{(T - T_1)}{(T_2 - T_1)}$$

$$T(V) = T_1 + \frac{(T_2 - T_1)(V - V_1)}{(V_2 - V_1)}$$

DUE TO SELF-HEATING, BY PASSING 30mA , TEMP CHANGES IF $P_D = 30\text{mW}/^{\circ}\text{C}$

$$\Delta T = \frac{P_D}{\frac{I^2 R}{P_D}} = \frac{(0.03)^2 \cdot 555.5}{0.03} = 16.665^{\circ}\text{C}$$

RESISTANCE TEMP DETECTORS (RTD)

↳ R OF MOST METALS Δ AS TEMP Δ

$$R[T] = R[T_0] (1 + \alpha_0 (T - T_0))$$

T = TEMP @ DESIRED RESISTANCE

$$R[T] = R @ T$$

RTD EX:

AN RTD HAS $\alpha_0 = 0.0037/^{\circ}\text{C}$ @ $T = 50^{\circ}\text{C}$

$R[T_0] = 500\Omega$. FIND R @ 80°C

$$R[T] = R[T_0] (1 + \alpha_0 (T - T_0)) = 500\Omega (1 + 0.0037^{\circ}\text{C} (80^{\circ}\text{C} - 50^{\circ}\text{C})) = 555.5\Omega$$

THERMISTOR

↳ SEMICONDUCTOR BASED TRANSDUCER

$$R[T] = R[T_0] e^{B \left(\frac{1}{T} - \frac{1}{T_0} \right)}$$


CALC R OF A THERMISTOR @ 100°C IF $R[0^{\circ}\text{C}] = 15\text{k}\Omega$

THE THERMISTOR TEMP COEF. = 2200K ($0^{\circ}\text{C} = 273\text{K}$)

$$R[T] = R[T_0] e^{B \left(\frac{1}{T} - \frac{1}{T_0} \right)} = (15000\Omega) e^{2200\text{K} \left(\frac{1}{323\text{K}} - \frac{1}{273\text{K}} \right)} = 2074.8\Omega$$

IC TEMP SENSORS

↳ VERY WELL LINEAR

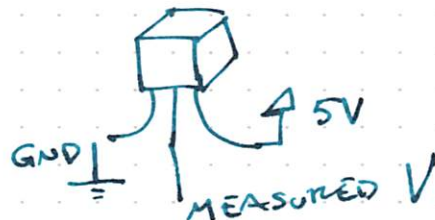

OPTICAL SENSORS

↳ PHOTO RESISTORS

↳ AN ANALOG DEVICE THAT MEASURES HOW BRIGHT OR DARK AN AREA IS

LED THEORY

$$\lambda = (1240/E) \text{ nm}$$

↳ IN GENERAL, 400-700 nm IS THE VISIBLE SPECTRUM

JAN 24, 2018

PHOTO TRANSDUCER

↳ OPB745 - IR LED w/ PHOTOTRANSISTOR

↳ PHOTOTRANSISTOR RESPONDS TO IR LED RADIATION ONLY WHEN A REFLECTIVE OBJECT PASSES IN FRONT OF THE FIELD OF VIEW

↳ LED OFF: NO I

↳ LED ON: I FLOWS

DISPLACEMENT TRANSDUCERS

POTENTIAL DISPLACEMENT SENSOR

↳ RESISTANCE Δ AS WIPER POSITION Δ

↳ PRO: CHEAP

↳ CON: WEARS OUT OVER TIME

↳ 3 TERMINALS B/C ONE IS TAP

LINEAR VARIABLE DIFFERENTIAL TRANSFORMER

↳ DISPLACEMENT SENSOR (ONLINE NOTES FOR FIGURE)

STRAIN GAGE

↳ Δ OF PLATINUM WIRE Δ BASED ON TENSION

↳ $R = \rho \frac{l}{A}$; $R = \Delta R$, ρ = RESISTIVITY, l = LENGTH, A = X-SECTION AREA

↳ EX: $\rho = 44.2 \times 10^{-6} \Omega \text{ cm}$, $l = 10 \text{ cm}$, $r = 0.01 \text{ mm}$

$$R = (44.2 \times 10^{-6} \Omega \text{ cm}) \frac{10 \text{ cm}}{\pi (0.01 \text{ mm})^2} = 141 \Omega$$

JAN 26, 2018

SCHMITT TRIGGER:

↳ USE HYSTERESIS BAND TO FIX NOISY SIGNALS

↳ ADD A HIGH & A LOW THRESHOLD

ADC

↳ RESOLUTION OF A/D: $\frac{V_{REF}}{(2^N - 1)}$

WHEATSTONE BRIDGE:

↳ CAN BE USED TO MEASURE UNKNOWN R

↳ COMBINES 2 VOLTAGE DIVIDERS


↳ EX: R_0 IS A SENSOR R_s

BAL $\rightarrow R_A = 1 \text{ k}\Omega$, $R_B = 2 \text{ k}\Omega$, $R_C = 3 \text{ k}\Omega$, $R_D = 6 \text{ k}\Omega$, $V_s = 10 \text{ V}$

$$V_- = V_+ = V \frac{R_D}{R_A + R_D} = 10 \text{ V} \left(\frac{2}{3} \right) = 6.667 \text{ V}$$


NON-BAL: $R_s = 6.6 \text{ k}\Omega$ (+10%)
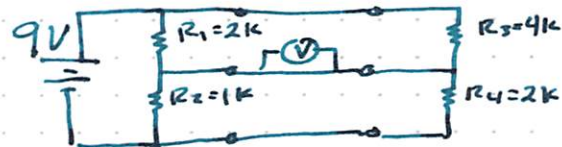
$$V_+ - V_- = V \frac{R_B}{R_A + R_B} - V \frac{R_D}{R_C + R_D} = 10 \left(\frac{2}{3} \right) - 10 \left(\frac{6600}{9000} \right) = -0.208 \text{ V}$$



JAN 31, 2018

OPERATIONAL AMPLIFIERS

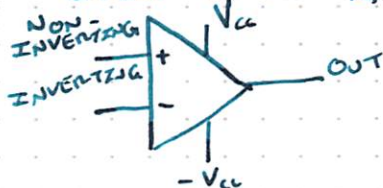

FROM KCL:

$$I_{o2} + I_{i2} + I_{p2} = I_{in}$$

$$V_o = A(V_p - V_n)$$

GAIN

IDEAL:

$$V_o = A(V_p - V_n)$$

$$\frac{V_o}{A} = 0$$

$$V_p = V_n$$

$$R_i = \infty$$

$$R_o = 0$$


FEEDBACK




NEGATIVE
↳ PART OF OUTPUT IS
RETURNED IN
OPPOSITE TO
SOURCE



POSITIVE
↳ OUTPUT SIGNAL
AIDS ORIGINAL

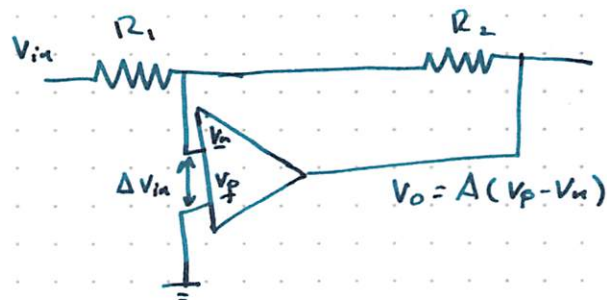


NON-INVERTING OP-AMP

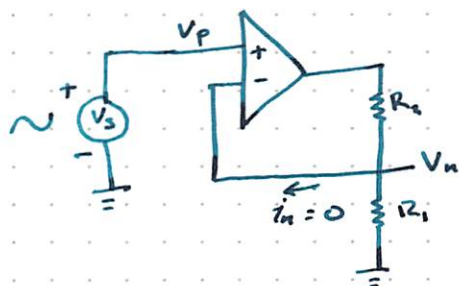


$$\begin{aligned} V_p &= V_s = V_n \\ V_n &= V_o \left(\frac{R_1}{R_1 + R_2} \right) \\ V_s &= V_o \left(\frac{R_1}{R_1 + R_2} \right) \\ V_o &= V_s \left(\frac{R_1 + R_2}{R_1} \right) \\ V_o &= V_s \left(1 + \frac{R_2}{R_1} \right) \end{aligned}$$

USUALLY RESTRICT $\{R_1, R_2\}$
TO BE BTWN $1k\Omega$ & $1M\Omega$

INVERTING OP-AMP

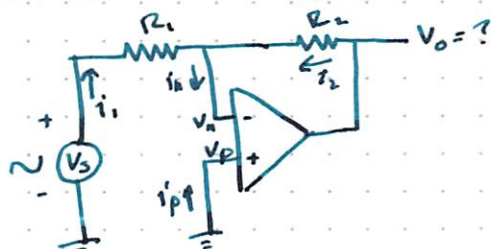

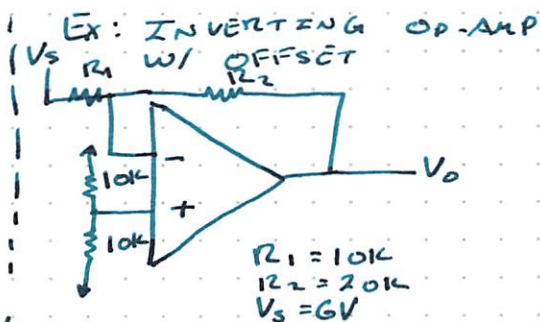
$$\begin{aligned} V_p &= V_n = 0 \\ i_1 &= \frac{V_s - V_n}{R_1} = \frac{V_s}{R_1} \\ i_2 &= \frac{V_o - V_n}{R_2} = \frac{V_o}{R_2} \end{aligned}$$



$$\begin{aligned} V_o &= -(V_s - V_n) \frac{R_2}{R_1} + V_n \\ &= -(6V - 5V) \frac{20k}{10k} + 5V \\ &= 3V \end{aligned}$$

FEB 02, 2018

VOLTAGE SUMMATION

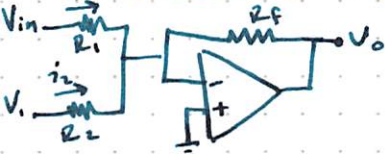

$$V_o = -V_{in} \frac{R_f}{R_1} - V_1 \frac{R_f}{R_2}$$

LEVEL SHIFTING & SCALING

IF $V_1 = -12V$, $R_f = R_1 = R_2 = 15k\Omega$

SOLVE FOR R_2 SO THAT WE SCALE SHIFT FROM OUR SENSOR RANGE
OF $-1.5V \rightarrow 3.5V$ TO $0V \rightarrow 5V$


$$V_o = V_{in} \frac{R_f}{R_1} - V_1 \frac{R_f}{R_2}$$

$$\begin{aligned} 0 &= -1.5 \frac{R_f}{R_1} - V_1 \frac{R_f}{R_2} \\ &= -1.5 + 12 \frac{15k}{R_2} \\ R_2 &= 120k\Omega \end{aligned}$$



$$\begin{aligned} 5 &= 3.5 \frac{R_f}{R_1} - V_1 \frac{R_f}{R_2} \\ R_2 &= 120k\Omega \end{aligned}$$

FEB 05, 2018

AMPLIFIER SIGNAL MODEL

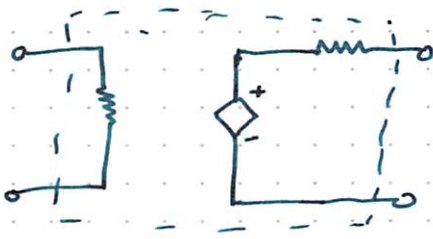

CASCADE AMPLIFIERS

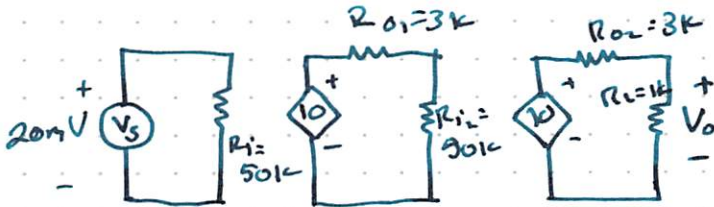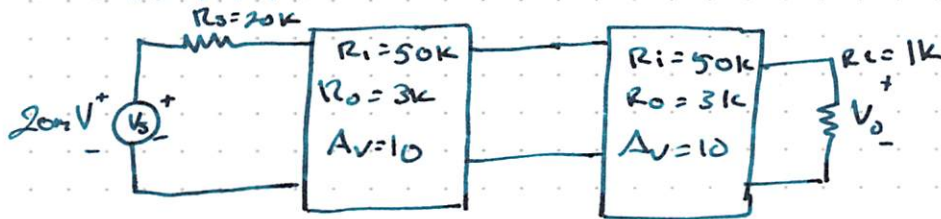

$$\frac{V_o}{V_s} = \frac{V_o}{V_{i2}} \cdot \frac{V_{i2}}{V_{i1}} \cdot \frac{V_{i1}}{V_s}$$

$$V_o = 10V_{i2} \left(\frac{R_L}{R_L + R_{o2}} \right); V_{i2} = 10V_{i1} \left(\frac{R_{i2}}{R_{i2} + R_{o1}} \right)$$

$$V_{i1} = V_s \left(\frac{R_{i1}}{R_{i1} + R_s} \right)$$

$$\frac{V_o}{V_s} = (2.5)(9.434)(0.7143) = 16.85$$

$$\frac{V_o}{V_{i2}} = 10 \left(\frac{R_L}{R_L + R_{o2}} \right) = 10 \left(\frac{1000}{4000} \right) = 2.5$$

$$\frac{V_{i2}}{V_{i1}} = 10 \left(\frac{50,000}{55,000} \right) = 9.434$$

$$\frac{V_{i1}}{V_s} = \frac{50,000}{70,000} = 0.7143$$

$$V_o = (20mV)(16.85) = 0.337V$$

NOISE

↳ THERMAL NOISE

$$N_{TH} = kTB$$

↳ N_{TH} = NOISE POWER IN WATTS

↳ $k = 1.38 \times 10^{-23}$ (BOLTZMANN'S CONSTANT)

↳ T = ABSOLUTE TEMP IN K

↳ B = BANDWIDTH (HZ)

↳ SHOT NOISE

$$I_N^2 = 2qI_{DC}B$$

LOW FREQ. NOISE

↳ DECREASES W/ FREQ INCREASE

FEB 01, 2018

IA TOTAL CMR

$$A_o = \frac{V_o}{V_{in}}$$
$$CMR = \frac{A_{DIFF}}{A_{CM}}$$

↑ HIGH
↑ LOW
↑ BAD

$$CMR_{TOTAL} = CMR_1 \cdot CMR_2$$

SLIDES FOR GIZANT
CIRCUIT

OPEN LOOP GAIN: NO EXTRA LOAD AFTER OP AMP

$$CMR_{1ST\ OP} = \frac{CMR_1 \cdot CMR_{OPAMP}}{CMR_1 + CMR_{OPAMP}}$$

EXAMPLE 2 FROM SLIDES

ADCs & DACs

- ↳ CHECK OUT NXP CUP CAP
- ↳ QUIZ 1 - FRZ, FEB 23 TEST

INTERFACING w/ THE REAL WORLD

- ↳ REAL WORLD HAS CONTINUOUS ANALOG SIGNALS
- ↳ MICROCONTROLLERS ONLY UNDERSTAND DISCRETE VALUES (BINARY)


ANALOG IN \rightarrow TRANSDUCER \rightarrow SIGNAL CONDITIONING \rightarrow SAMPLING & HOLD \rightarrow ADC
SPECS:

- RESOLUTION
- CONVERSION TIME
- ACCURACY

ACCURACY

↳ MORE BITS \rightarrow MORE FIDELITY

DAC CIRCUIT

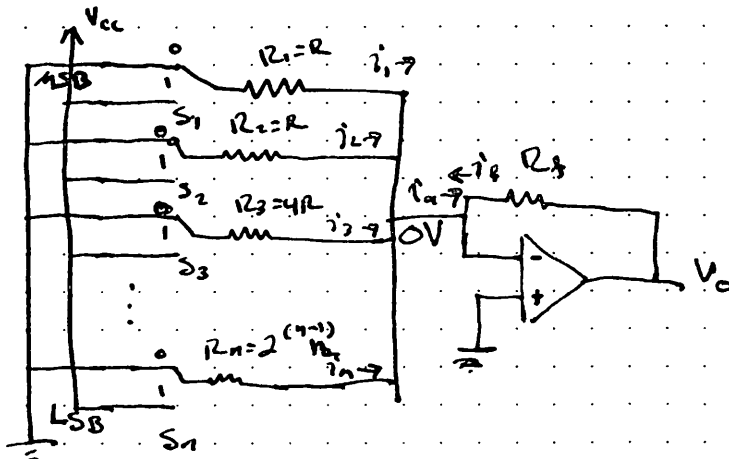

IF ALL SWITCHES = 1

$$V_o = -V_{cc} \left(\frac{R_f}{R_1 \parallel R_2 \parallel \dots \parallel R_n} \right)$$

$$i_a = \sum_{i=1}^n \frac{a_i V_{cc}}{2^{i-1} R}$$

WHERE n = # OF BITS

a_i = EITHER 1 or 0 BASED ON BIT

~~PROG~~

$$V_o - V_n = V_o = -i_a R_f$$

$$\begin{aligned} V_o &= -i_a R_f \\ &= -R_f \left(\sum_{i=1}^n \frac{a_i V_{cc}}{2^{i-1} R} \right) \end{aligned}$$

FEB 12, 2018

7

PROBLEMS: MORE BITS \rightarrow LARGER RESISTORS
↳ LOW CURRENT
↳ HARD TO MANUFACTURE



EXAMPLE:

SOLVE FOR R_f FOR 4-BITS LADDER & $R = 100\Omega$
 WANT TO MAP 0-15 DIGITAL VALUES FOR
 0-15V OUTPUT VALUES. LOGIC 1 = 5V

$$V_o = \frac{-R_f V_{cc}}{R} \left(\sum_{i=1}^n \frac{a_i}{2^{i-1}} \right)$$


FEB 12, 2018 (ΔGAIN...

R-2R RESISTANCE LADDER

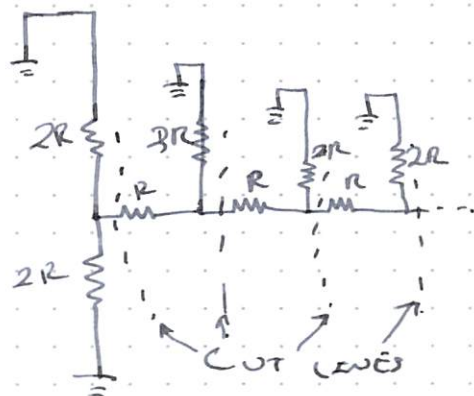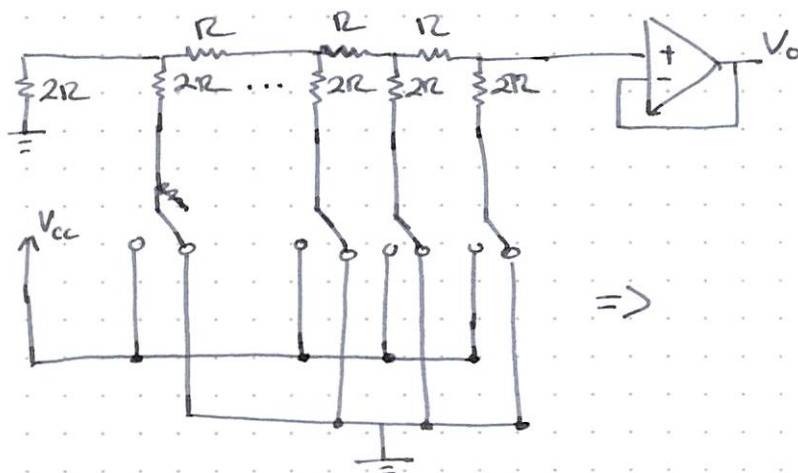


$$V_{OUT} = V_{cc} \sum_{i=1}^n \frac{a_i}{2^i}$$


USE THEVENIN TO
SIMPLIFY

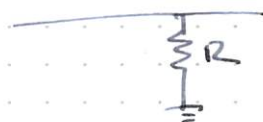

FEB 14, 2018
 ADC,
 SERVO ADC

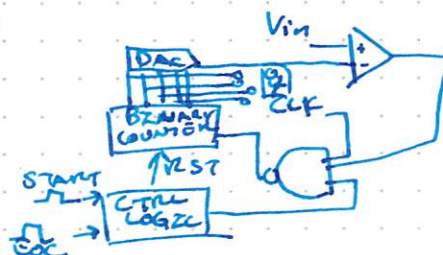

SUCCESSIVE APPROX

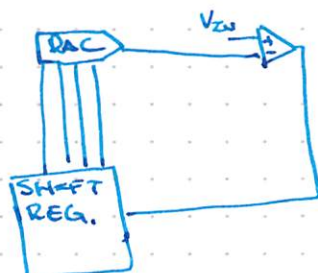

CHECKS BIT-BY-BIT
 TO CONFIRM ANALOG → VOLTAGE

$$IS \quad V_{in} \geq 10 \left(\sum \frac{1}{2^n} \right)$$

DSP - FEB 16, 2018
IDE

ADC SPECIFICATIONS

↳ CONVERSION TIME, Δt

$$\Delta t = \frac{1}{2f_{\max}}$$

↳ RESOLUTION, EITHER # OF BITS n
OR STEP VOLTAGE ΔV

↳

↳

EXAMPLE: A THERMISTOR IS USED TO MEASURE TEMPERATURE FROM 0°C TO 100°C . YOU WANT TO REPORT TEMP W/ A RESOLUTION OF $\pm 1^\circ\text{C}$. IT PRODUCES $0 \rightarrow 5\text{V}$ OVER THE TEMP RANGE W/ 5mV OF NOISE.

• SPECIFY n BASED ON a) DYNAMIC RANGE
b) REQUIRED RESOLUTION

$$\begin{aligned} 2^n &\geq \frac{V_{\max}}{V_{\text{NOISE}}} \\ &\geq \frac{5\text{V}}{5\text{mV}} \\ &\geq 1000 \\ n &\text{ MUST BE } \geq 10 \end{aligned}$$

EX: MAX CONVERSION TIMES FOR AN 8-BIT ADC TO DIGITIZE THE FOLLOWING SIGNALS?

↳ 1 Hz SIN $\rightarrow \Delta t = \frac{1}{2f_{\max}} = \frac{1}{2} = 0.5\text{s}$

↳ 1 kHz SIN

↳ 1 MHz SIN

$$\frac{1}{2000} = 0.5\text{ms}$$

$$\frac{1}{2000000} = 0.5\mu\text{s}$$

↳ MAX APERTURE TIME

$$\text{↳ } 1\text{ Hz} \rightarrow t_{\text{AP}} = \frac{1}{2\pi f_{\max} 2^n} = \frac{1}{2\pi (1) 2^8} = 0.62\text{ms}$$

↳ 1 kHz

↳ 1 MHz

$$= \frac{1}{2\pi (1000) 2^8} = 0.62\mu\text{s}$$

$$= \frac{1}{2\pi (1000000) 2^8} = 0.62\text{ns}$$

GIVEN A $+5V$ P-P SIGNAL W/ $5mV$ P-P NOISE,
 $f_{max} = 3kHz$ SPECIFY:

↳ DYNAMIC RANGE: $\frac{V_{max}}{V_{noise}} = \frac{10V}{5mV} = 2000$


↳ $2^n \geq \frac{V_{max}}{V_{noise}} = 2000$

$\therefore n \geq 11$

↳ MAX CONVERSION TIME: $\Delta t = \frac{1}{2f_{max}}$
 $= \frac{1}{2(3000)} = 170\mu s$

↳ CUTOFF FREQ FOR AA FILTER: $3kHz = f_{max}$

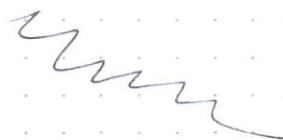↳ APERTURE TIME: $t_{AP} = \frac{1}{2\pi f_{max} 2^n} = \frac{1}{2\pi (3000) 2^{11}} = 26ns$




FEB 19, 2018 - IDE

SWITCHING


- ↳ MICROCONTROLLERS ARE GOOD AT TURNING THINGS ON/OFF
- ↳ WE NEED TO AMPLIFY SIGNALS TO DRIVE MORE POWERFUL STUFF

RELAYS

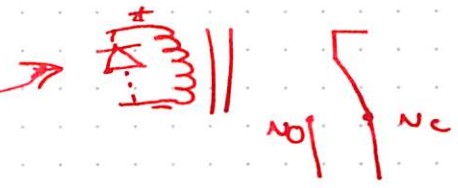- ↳ HIGH POWER ELECTROMECHANICAL SWITCH
- ↳ PROTECTION DIODE 
- ↳ WHEN THE RELAY IS SWITCHED OFF, THE SUDDEN FIELD COLLAPSE CAUSES A GIANT VOLTAGE SPOKE
- ↳ DIODE ALLOWS PATH TO HANDLE THE CURRENT
- ↳ CAN CASCADE RELAYS
- ↳ SMALLER ACTIVATES LARGER

FLASH ADC
 ↳ USES 1 COMPARATOR PER BIT
 ↳ FAST
 ↳ HIGH QUALITY

DUAL SLOPE

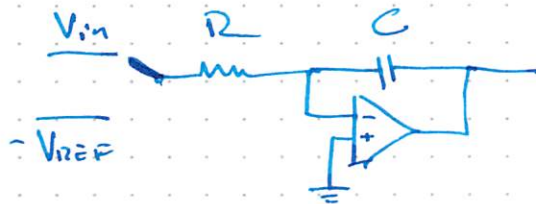

FEB 26, 2018

SWITCHES:

- ↳ MULTIPLE SWITCHES:
 - ↳ PARALLEL - ANY SWITCH TRIPS, THEY ALL TRIP
 - ↳ SERIES - ALL NEED TO TRIP SIMULTANEOUSLY
 - ↳ USE Σ NETWORK TO FORM A VOLTAGE DIVIDER

HYDRAULIC V. ELECTRIC V. PNEUMATIC

- ↳ ELECTRIC - ACCURACY OR CONTINUOUS MOVEMENT
- ↳ ~~HEAVY~~ ~~LOAD~~ HYDRAULIC - HEAVY LOADS / SMOOTH MOVEMENT
- ↳ PNEUMATIC - FAST
 - ↳ COMPRESSED AIR IS HARD
 - ↳ CAN'T DO HEAVY LOADS

FEB 28, 2018

MOTORS

- ↳ A MOTOR IS A TRANSDUCER
- ↳ RATED VOLTAGE IS MOST EFFICIENT

READ SLIDES

EX: WE WANT A 2-WHEELED, 2kg CAR TO GO UP A 30° SLOPE @ $V = 1/2$ ft/s
 WHEEL DIAM: 3", $\mu = 0.7$ $T = ?$ $RPM = ?$

$$F_T = F_W + F_f$$

$$F_W = mg \sin \theta$$

$$F_f = \mu mg \cos \theta$$

$$F_T = F_W + F_f$$

$$= mg (\sin \theta + \mu \cos \theta)$$

$$= \left(\frac{2}{2}\right) (9.81 \text{ m/s}^2) (52 \text{ N} (30^\circ) + 0.7 \sin (30^\circ))$$

$$= 10.89 \text{ N}$$

$$T = F \cdot r$$

$$= (10.89 \text{ N}) (1.5 \text{ in}) \left(\frac{2.54 \text{ cm/in}}{100 \text{ cm}}\right) = 0.4149 \text{ Nm}$$

NECESSARY TORQUE

MAR 02, 2014

MORE MOTORS:

MAR 05, 2014

STEPPER MOTORS

- ↳ USE MAGNETS TO MOVE MOTOR TEETH BY-TEETH
- ↳ PRECISE MOVEMENT, LOW TORQUE

UNIPOLAR & BIPOLAR STEPPER MOTORS

↓
MORE COMMON
4 SETS OF WINDINGS

↓
MORE SPEED & TORQUE
2 SETS OF WINDINGS


MAR 07, 2014

ENCODERS

- ↳ ABSOLUTE POSITION
- ↳ EXACT DEGREE OF WHEEL
- ↳ INCREMENTAL
- ↳ TELLS YOU WHEN YOU'VE ROTATED X-DEGREES

ENCODERS REQUIRE HYSTERESIS BAND


PASSIVE FILTER DESIGN
LOW PASS:

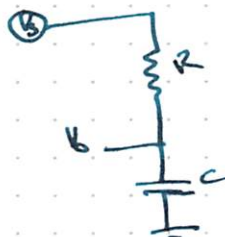

MAR 09, 2014

MAGNITUDE: $\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{1 + (wRC)^2}}$

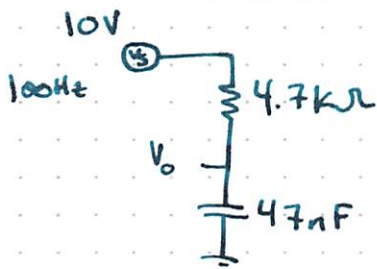PHASE: $\angle \left(\frac{V_{out}}{V_{in}} \right) = -\tan^{-1} \left(\frac{wRC}{1} \right)$



$$V_o = V_s \frac{X_c}{\sqrt{R^2 + X_c^2}} = 10V \frac{33863\Omega}{\sqrt{(4700)^2 + (33863)^2}} = 9.9V$$


$$X_c = \frac{1}{2\pi(f)(C)} = \frac{1}{2\pi(100Hz)(47E-9)} = 33863\Omega$$

$$w = 2\pi f$$
$$f = 100; 10,000$$

$$w = 628; 62832$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{1 + (wRC)^2}} = \frac{1}{\sqrt{1 + ((628)(4700)(47E-9))^2}} = 0.99$$

CALCULATING f_c & PHASE SHIFT

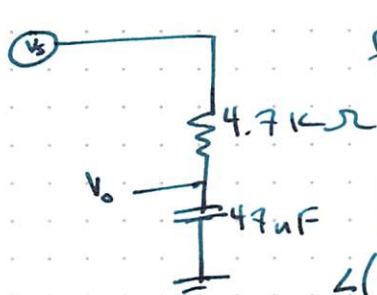

$$f_c = \frac{1}{2\pi RC} = \frac{1}{2\pi(4700)(47 \times 10^{-6})} = 720 \text{ Hz}$$

$$\omega = 2\pi f = 4524$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{1 + ((4524)(4700)(47 \times 10^{-6}))^2}} = 0.707$$

$$\angle \left(\frac{V_{out}}{V_{in}} \right) = -\tan^{-1}(\omega RC) = -45^\circ$$

$$V_o = V_s \frac{X_c}{\sqrt{R^2 + X_c^2}} ; X_c = \frac{1}{\omega C} = \frac{1}{(4524)(47 \times 10^{-6})} = 4703 \Omega$$

$$= 10 \frac{4703}{\sqrt{(4700)^2 + (4703)^2}} = \cancel{7.07} \text{ V}$$

HIGH PASS FILTER




$$V_o = V_s \frac{R}{R + X_c}$$

$$V_o = V_s \frac{R}{R + \frac{1}{\omega C}}$$

$$V_o = V_s = \frac{\omega RC}{\omega RC + 1}$$
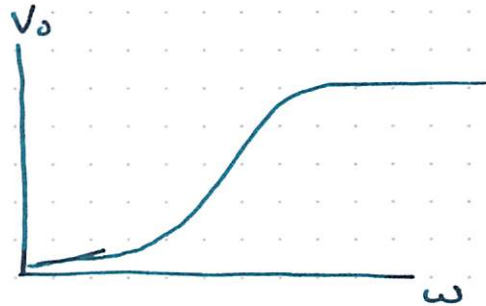
$$X_c = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$



$$\frac{V_{out}}{V_{in}} = \frac{j\omega RC}{j\omega RC + 1}$$

$$\text{MAG: } \left| \frac{V_{out}}{V_{in}} \right| = \frac{\omega RC}{\sqrt{1 + (\omega RC)^2}}$$


$$\text{PHASE: } \angle \frac{V_{out}}{V_{in}} = \tan^{-1} \left(\frac{1}{\omega RC} \right)$$

$$f_c = \frac{1}{2\pi RC}$$

MAR 19, 2018

EXAM NEXT FRIDAY

EX:

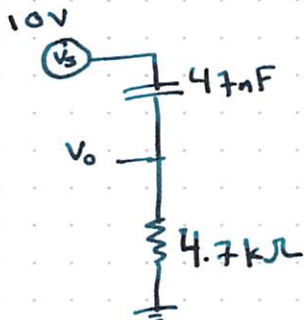

CALC f_c

CALC MAG, PHASE SHIFT, & V_o @ 720 Hz

$$f_c = \frac{1}{2\pi RC} = 720 \text{ Hz} ; \omega = 2\pi f_c = 4524 \text{ RAD}$$


$$\left| \frac{V_o}{V_i} \right| = \frac{\omega RC}{\sqrt{1 + (\omega RC)^2}} = 0.707$$

$$\angle (V_{out}/V_{in}) = \tan^{-1}(\omega RC) = 45^\circ$$

$$V_o = V_s \frac{R}{\sqrt{R^2 + X_c^2}} = 10 \frac{4700}{\sqrt{(4700)^2 + (4703)^2}} ; X_c = \frac{1}{\omega C} = 4703 \Omega$$

$$= 7.07 \text{ V}$$


HIGHER ORDER FILTERS

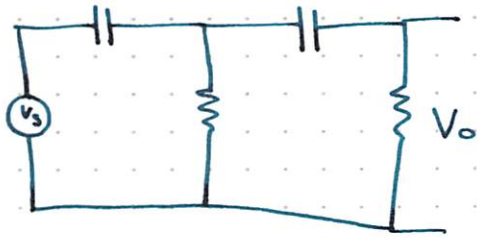

DIFFERENTIATOR CIRCUIT

HIGHER FREQ \rightarrow EDGE ENHANCEMENT


BAND PASS

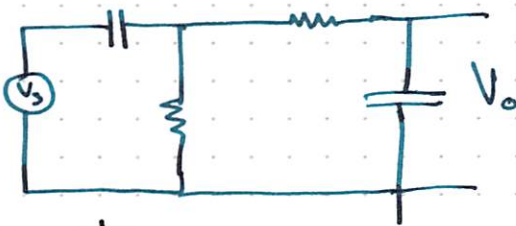

$$f_L = \frac{1}{2\pi RC_L}$$

$$f_H = \frac{1}{2\pi RC_H}$$

$$f_{center} = f_r = \sqrt{f_L f_H}$$

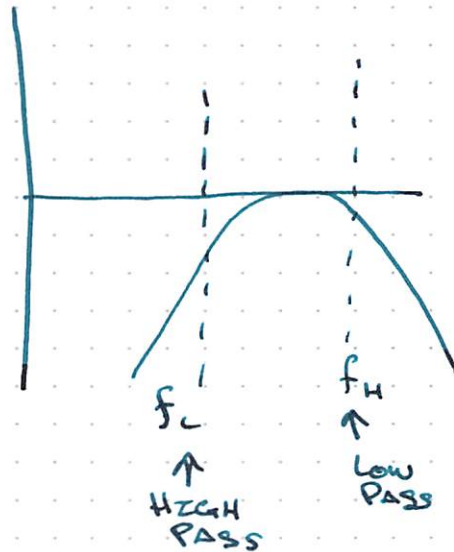

ACTIVE FILTERS

EX: NON-INVERTING ACTIVE LOW-PASS FILTER

$A_{DC} = 10$; $f_c = 159 \text{ Hz}$; INPUT IMPEDANCE = $10 \text{ k}\Omega$



$$A_{DC} = 1 + \frac{R_2}{R_1}$$

$$R_2 = R_1 (A_{DC} - 1)$$

ASSUME $R_1 = 1 \text{ k}\Omega$

$$R_2 = (1000)(9) = 9 \text{ k}\Omega$$

$$C = \frac{1}{2\pi R f_c} = \frac{1}{2\pi (10 \text{ k}) (159)}$$

$$= 100 \text{ nF}$$


INTRO

- ↳ WHY WIDEBAND GAP MATERIALS?
- ↳ INTRINSIC PROPERTIES
- ↳ LARGE ENERGY GAP
- ↳ CAN HANDLE HIGH CURRENT DENSITY
- ↳ HIGHER V OPERATION
- ↳ SMALLER COMPONENTS

↳ SiC/GaN

MAR 21, 2018

FILTER IMPROVEMENTS

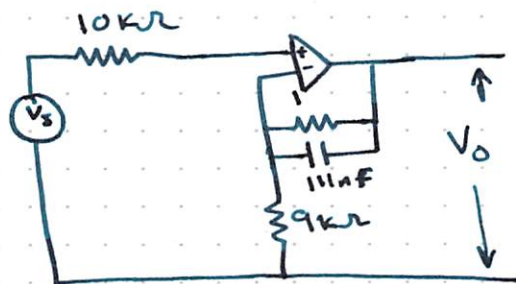

SALLEN-KEY 2ND ORDER LOW PASS ACTIVE FILTER

EX: 1ST ORDER HIGH-PASS NON-INV. OP-AMP
W/ A PASS BAND $A_{DC} = 2$, $C = 10nF$, $f_c = 1kHz$

$$R = \frac{1}{2\pi f_c C} = 15.92k\Omega$$

$$A_{DC} = 1 + \frac{R_2}{R_1}$$
$$2 = 1 + \frac{R_2}{R_1}$$

$$R_2 = R_1 (10k\Omega)$$

CHOICE,
10K EASIER?

~~MAR 23, 2018~~ APR 2, 2018

DIGITAL FILTERING

- ↳ TYPICALLY IN SOFTWARE

DIGITAL FILTER FOR CAR (UNEVEN LIGHTING IN GYM)

AVERAGING FILTER CAN SMOOTH CAMERA NOISE.

DERIVATIVE FILTER

↳


- 1) NORMALIZE
 - ↳ COMPENSATE FOR LIGHTING
- 2) BLUR → REMOVE NOISE
- 3) DERIV. W/ ABS
- 4) FIND PEAKS & CENTER TRACK

BJT EX. 2

$$I_B = \frac{I_C}{\beta} = \frac{4\text{mA}}{270} = 15\mu\text{A}$$

$$\text{USE 3) } \frac{V_{CE} - V_{BE}}{I_B} = \frac{7.5\text{V} - 0.7\text{V}}{15\mu\text{A}} = 453\text{k}\Omega = R_B$$
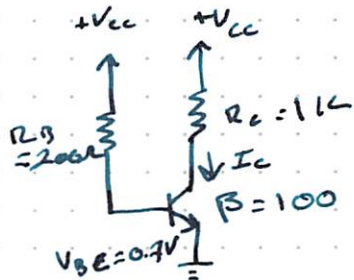
$$\text{USE 2) } R_C = \frac{V_{CC} - V_{CE}}{I_B + I_C} = \frac{15 - 7.5}{15\mu\text{A} + 4\text{mA}} = 1.87\text{k}\Omega$$



$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{15 - 0.7}{200} = 71.5\text{mA}$$

$$I_C = \beta I_B = 7.15\text{A} \quad \star \leftarrow \text{CAN'T WORK IN SATURATION}$$

$$V_{CE} = V_{CC} - I_C R_C = 15\text{V} - (7.15\text{A})(1\text{k}\Omega) = -7135\text{V}$$

SATURATION

WHAT ARE I_B & I_C @ EDGE OF SATURATION

ASSUME $V_{CE} = 0.2\text{V}$ WHEN OPERATING IN SATURATION

$$V_{CC} = V_{CE} + I_C R_C$$

$$I_C = \frac{V_{CC} - V_{CE}}{R_C} = \frac{15 - 0.2}{1000} = 14.8\text{mA}$$